

21.1 (a) $\Delta V_{\max} = \sqrt{2}(\Delta V_{\text{rms}}) = \sqrt{2}(100 \text{ V}) = \boxed{141 \text{ V}}$

(b) $I_{\text{rms}} = \frac{\Delta V_{\text{rms}}}{R} = \frac{100 \text{ V}}{5.00 \Omega} = \boxed{20.0 \text{ A}}$

(c) $I_{\max} = \frac{\Delta V_{\max}}{R} = \frac{141 \text{ V}}{5.00 \Omega} = \boxed{28.3 \text{ A}}$ or $I_{\max} = \sqrt{2}I_{\text{rms}} = \sqrt{2}(20.0 \text{ A}) = \boxed{28.3 \text{ A}}$

(d) $\mathcal{P}_{\text{av}} = I_{\text{rms}}^2 R = (20.0 \text{ A})^2 (5.00 \Omega) = 2.00 \times 10^3 \text{ W} = \boxed{2.00 \text{ kW}}$

21.2 $\mathcal{P}_{\text{av}} = I_{\text{rms}}^2 R = \left(\frac{I_{\max}}{\sqrt{2}}\right)^2 R = \frac{1}{2} \left[\frac{\Delta V_{\max}}{R}\right]^2 R = \frac{(\Delta V_{\max})^2}{2R}$, so $R = \frac{(\Delta V_{\max})^2}{2\mathcal{P}_{\text{av}}}$

(a) If $\mathcal{P}_{\text{av}} = 75.0 \text{ W}$, then $R = \frac{(170 \text{ V})^2}{2(75.0 \text{ W})} = \boxed{193 \Omega}$

(b) If $\mathcal{P}_{\text{av}} = 100 \text{ W}$, then $R = \frac{(170 \text{ V})^2}{2(100 \text{ W})} = \boxed{145 \Omega}$

21.5 The total resistance (series connection) is $R_{\text{eq}} = R_1 + R_2 = 8.20 \Omega + 10.4 \Omega = 18.6 \Omega$, so the current in the circuit is

$$I_{\text{rms}} = \frac{\Delta V_{\text{rms}}}{R_{\text{eq}}} = \frac{15.0 \text{ V}}{18.6 \Omega} = 0.806 \text{ A}$$

The power to the speaker is then $\mathcal{P}_{\text{av}} = I_{\text{rms}}^2 R_{\text{speaker}} = (0.806 \text{ A})^2 (10.4 \Omega) = \boxed{6.76 \text{ W}}$

21.6 (a) $\Delta V_{\max} = 150 \text{ V}$, so $\Delta V_{\text{rms}} = \frac{\Delta V_{\max}}{\sqrt{2}} = \frac{150 \text{ V}}{\sqrt{2}} = \boxed{106 \text{ V}}$

(b) $f = \frac{\omega}{2\pi} = \frac{377 \text{ rad/s}}{2\pi} = \boxed{60.0 \text{ Hz}}$

(c) At $t = (1/120) \text{ s}$, $v = (150 \text{ V})\sin[(377 \text{ rad/s})(1/120 \text{ s})] = (150 \text{ V})\sin(\pi \text{ rad}) = \boxed{0}$

(d) $I_{\max} = \frac{\Delta V_{\max}}{R} = \frac{150 \text{ V}}{50.0 \Omega} = \boxed{3.00 \text{ A}}$

21.30 (a) $X_L = 2\pi fL = 2\pi(60.0 \text{ Hz})(0.100 \text{ H}) = 37.7 \ \Omega$

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(60.0 \text{ Hz})(200 \times 10^{-6} \text{ F})} = 13.3 \ \Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{(20.0 \ \Omega)^2 + (37.7 \ \Omega - 13.3 \ \Omega)^2} = 31.6 \ \Omega$$

$$\mathcal{P}_{\text{av}} = I_{\text{rms}}^2 R = \left(\frac{I_{\text{max}}}{\sqrt{2}}\right)^2 R = \frac{1}{2} \left(\frac{\Delta V_{\text{max}}}{Z}\right)^2 R = \frac{1}{2} \left(\frac{100 \text{ V}}{31.6 \ \Omega}\right)^2 (20.0 \ \Omega) = \boxed{100 \text{ W}}$$

$$\text{and power factor} = \cos \phi = \frac{\mathcal{P}_{\text{av}}}{\Delta V_{\text{rms}} I_{\text{rms}}} = \frac{I_{\text{rms}}^2 R}{\Delta V_{\text{rms}} I_{\text{rms}}} = \left(\frac{I_{\text{rms}}}{\Delta V_{\text{rms}}}\right) R = \frac{R}{Z} = \frac{20.0 \ \Omega}{31.6 \ \Omega} = \boxed{0.633}$$

(b) The same calculations as shown in Part (a) above, with $f = 50.0 \text{ Hz}$, give

$$X_L = 31.4 \ \Omega, \quad X_C = 15.9 \ \Omega, \quad Z = 25.3 \ \Omega, \quad \mathcal{P}_{\text{av}} = \boxed{156 \text{ W}} \quad \text{and power factor} = \boxed{0.790}$$

21.33 The resonance frequency of the circuit should match the broadcast frequency of the station.

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \text{ gives } L = \frac{1}{4\pi^2 f_0^2 C},$$

$$\text{or } L = \frac{1}{4\pi^2 (88.9 \times 10^6 \text{ Hz})^2 (1.40 \times 10^{-12} \text{ F})} = 2.29 \times 10^{-6} \text{ H} = \boxed{2.29 \ \mu\text{H}}$$

21.34 (a) At resonance, $X_L = X_C$ so the impedance will be

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{R^2 + 0} = R = \boxed{15 \Omega}$$

(b) When $X_L = X_C$, we have $2\pi fL = \frac{1}{2\pi fC}$ which yields

$$f = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(0.20 \text{ H})(75 \times 10^{-6} \text{ F})}} = \boxed{41 \text{ Hz}}$$

(c) The current is a maximum at resonance where the impedance has its minimum value of $Z = R$.

(d) At $f = 60 \text{ Hz}$, $X_L = 2\pi(60 \text{ Hz})(0.20 \text{ H}) = 75 \Omega$, $X_C = \frac{1}{2\pi(60 \text{ Hz})(75 \times 10^{-6} \text{ F})} = 35 \Omega$,

$$\text{and } Z = \sqrt{(15 \Omega)^2 + (75 \Omega - 35 \Omega)^2} = 43 \Omega$$

$$\text{Thus, } I_{\text{rms}} = \frac{\Delta V_{\text{rms}}}{Z} = \frac{(\Delta V_{\text{max}}/\sqrt{2})}{Z} = \frac{150 \text{ V}}{\sqrt{2}(43 \Omega)} = \boxed{2.5 \text{ A}}$$

21.38 (a)
$$\Delta V_{2,\text{rms}} = \frac{N_2}{N_1}(\Delta V_{1,\text{rms}})$$

$$\text{so } N_2 = N_1 \left(\frac{\Delta V_{2,\text{rms}}}{\Delta V_{1,\text{rms}}} \right) = (240 \text{ turns}) \left(\frac{9.0 \text{ V}}{120 \text{ V}} \right) = \boxed{18 \text{ turns}}$$

(b) For an ideal transformer, $(\mathcal{P}_{\text{av}})_{\text{input}} = (\mathcal{P}_{\text{av}})_{\text{output}} = (\Delta V_{2,\text{rms}})I_{2,\text{rms}}$

$$\text{Thus, } (\mathcal{P}_{\text{av}})_{\text{input}} = (9.0 \text{ V})(0.400 \text{ A}) = \boxed{3.6 \text{ W}}$$

$$21.42 \quad R_{line} = (4.50 \times 10^{-4} \text{ } \Omega/\text{m})(6.44 \times 10^5 \text{ m}) = 290 \text{ } \Omega$$

(a) The power transmitted is $(\mathcal{P}_{av})_{transmitted} = (\Delta V_{rms}) I_{rms}$

$$\text{so } I_{rms} = \frac{(\mathcal{P}_{av})_{transmitted}}{\Delta V_{rms}} = \frac{5.00 \times 10^6 \text{ W}}{500 \times 10^3 \text{ V}} = 10.0 \text{ A}$$

$$\text{Thus, } (\mathcal{P}_{av})_{loss} = I_{rms}^2 R_{line} = (10.0 \text{ A})^2 (290 \text{ } \Omega) = 2.90 \times 10^4 \text{ W} = \boxed{29.0 \text{ kW}}$$

(b) The power input to the line is

$$(\mathcal{P}_{av})_{input} = (\mathcal{P}_{av})_{transmitted} + (\mathcal{P}_{av})_{loss} = 5.00 \times 10^6 \text{ W} + 2.90 \times 10^4 \text{ W} = 5.03 \times 10^6 \text{ W}$$

and the fraction of input power lost during transmission is

$$fraction = \frac{(\mathcal{P}_{av})_{loss}}{(\mathcal{P}_{av})_{input}} = \frac{2.90 \times 10^4 \text{ W}}{5.03 \times 10^6 \text{ W}} = \boxed{0.00580 \text{ or } 0.580\%}$$