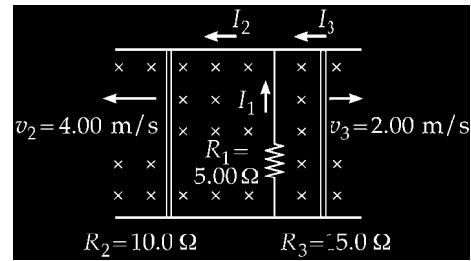


Chapter 31

**P31.31**  
diagram:

Name the currents as shown in the



**FIG. P31.31**

Left loop:  
 $+Bdv_2 - I_2R_2 - I_1R_1 = 0$

Right loop:  
 $+Bdv_3 - I_3R_3 + I_1R_1 = 0$

At the junction:  $I_2 = I_1 + I_3$

Then,  $Bdv_2 - I_1R_2 - I_3R_2 - I_1R_1 = 0$

$$I_3 = \frac{Bdv_3}{R_3} + \frac{I_1R_1}{R_3}.$$

So,  $Bdv_2 - I_1(R_1 + R_2) - \frac{Bdv_3R_2}{R_3} - \frac{I_1R_1R_2}{R_3} = 0$

$$I_1 = Bd \left( \frac{v_2R_3 - v_3R_2}{R_1R_2 + R_1R_3 + R_2R_3} \right) \text{ upward}$$

$$I_1 = (0.0100 \text{ T})(0.100 \text{ m}) \left[ \frac{(4.00 \text{ m/s})(15.0 \Omega) - (2.00 \text{ m/s})(10.0 \Omega)}{(5.00 \Omega)(10.0 \Omega) + (5.00 \Omega)(15.0 \Omega) + (10.0 \Omega)(15.0 \Omega)} \right] = \boxed{145 \mu\text{A}} \text{ upward.}$$

**P31.41** (a)  $\Phi_B = BA \cos \theta = BA \cos \omega t = (0.800 \text{ T})(0.0100 \text{ m}^2) \cos 2\pi(60.0)t = \boxed{(8.00 \text{ mT} \cdot \text{m}^2) \cos(377t)}$

(b)  $\varepsilon = -\frac{d\Phi_B}{dt} = \boxed{(3.02 \text{ V}) \sin(377t)}$

(c)  $I = \frac{\varepsilon}{R} = \boxed{(3.02 \text{ A}) \sin(377t)}$

(d)

(e) so