

**P33.10** At 50.0 Hz,  $X_L = 2\pi(50.0 \text{ Hz})L = 2\pi(50.0 \text{ Hz})\left(\frac{X_L|_{60.0 \text{ Hz}}}{2\pi(60.0 \text{ Hz})}\right) = \frac{50.0}{60.0}(54.0 \Omega) = 45.0 \Omega$

$$I_{\max} = \frac{\Delta V_{\max}}{X_L} = \frac{\sqrt{2}(\Delta V_{\text{rms}})}{X_L} = \frac{\sqrt{2}(100 \text{ V})}{45.0 \Omega} = \boxed{3.14 \text{ A}}$$

**P33.15**  $I_{\max} = \sqrt{2}I_{\text{rms}} = \frac{\sqrt{2}(\Delta V_{\text{rms}})}{X_C} = \sqrt{2}(\Delta V_{\text{rms}})2\pi fC$

(a)  $I_{\max} = \sqrt{2}(120 \text{ V})2\pi(60.0/\text{s})(2.20 \times 10^{-6} \text{ C/V}) = \boxed{141 \text{ mA}}$

(b)  $I_{\max} = \sqrt{2}(240 \text{ V})2\pi(50.0/\text{s})(2.20 \times 10^{-6} \text{ F}) = \boxed{235 \text{ mA}}$

**P33.21** (a)  $X_L = \omega L = 2\pi(50.0 \text{ s}^{-1})(250 \times 10^{-3} \text{ H}) = \boxed{78.5 \Omega}$

(b)  $X_C = \frac{1}{\omega C} = \left[2\pi(50.0 \text{ s}^{-1})(2.00 \times 10^{-6} \text{ F})\right]^{-1} = \boxed{1.59 \text{ k}\Omega}$

(c)  $Z = \sqrt{R^2 + (X_L - X_C)^2} = \boxed{1.52 \text{ k}\Omega}$

(d)  $I_{\max} = \frac{\Delta V_{\max}}{Z} = \frac{210 \text{ V}}{1.52 \times 10^3 \Omega} = \boxed{138 \text{ mA}}$

(e)  $\phi = \tan^{-1}\left[\frac{X_L - X_C}{R}\right] = \tan^{-1}(-10.1) = \boxed{-84.3^\circ}$

**P33.26**  $X_C = \frac{1}{\omega C} = \frac{1}{2\pi(50.0)(65.0 \times 10^{-6})} = 49.0 \Omega$

$$X_L = \omega L = 2\pi(50.0)(185 \times 10^{-3}) = 58.1 \Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{(40.0)^2 + (58.1 - 49.0)^2} = 41.0 \Omega$$

$$I_{\max} = \frac{\Delta V_{\max}}{Z} = \frac{150}{41.0} = 3.66 \text{ A}$$

(a)  $\Delta V_R = I_{\max}R = (3.66)(40) = \boxed{146 \text{ V}}$

(b)  $\Delta V_L = I_{\max}X_L = (3.66)(58.1) = 212.5 = \boxed{212 \text{ V}}$

(c)  $\Delta V_C = I_{\max}X_C = (3.66)(49.0) = 179.1 \text{ V} = \boxed{179 \text{ V}}$

(d)  $\Delta V_L - \Delta V_C = 212.5 - 179.1 = \boxed{33.4 \text{ V}}$

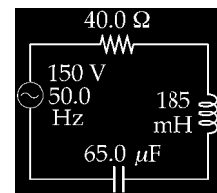


FIG. P33.26

P33.32

$$\text{or } (X_L - X_C) = \sqrt{Z^2 - R^2}$$

P33.40  $L = 20.0 \text{ mH}$ ,  $C = 1.00 \times 10^{-7}$ ,  $R = 20.0 \Omega$ ,  $\Delta V_{\text{max}} = 100 \text{ V}$

(a) The resonant frequency for a series  $-RLC$  circuit is  $f = \frac{1}{2\pi} \sqrt{\frac{1}{LC}} = \boxed{3.56 \text{ kHz}}$ .

(b) At resonance,  $I_{\text{max}} = \frac{\Delta V_{\text{max}}}{R} = \boxed{5.00 \text{ A}}$ .

(c) From Equation 33.38,  $Q = \frac{\omega_0 L}{R} = \boxed{22.4}$ .

(d)  $\Delta V_{L, \text{max}} = X_L I_{\text{max}} = \omega_0 L I_{\text{max}} = \boxed{2.24 \text{ kV}}$

P33.46 (a)  $(\Delta V_{2, \text{rms}}) = \frac{N_2}{N_1} (\Delta V_{1, \text{rms}})$   $N_2 = \frac{(2\,200)(80)}{110} = \boxed{1\,600 \text{ windings}}$

(b)  $I_{1, \text{rms}} (\Delta V_{1, \text{rms}}) = I_{2, \text{rms}} (\Delta V_{2, \text{rms}})$   $I_{1, \text{rms}} = \frac{(1.50)(2\,200)}{110} = \boxed{30.0 \text{ A}}$

(c)  $0.950 I_{1, \text{rms}} (\Delta V_{1, \text{rms}}) = I_{2, \text{rms}} (\Delta V_{2, \text{rms}})$   $I_{1, \text{rms}} = \frac{(1.20)(2\,200)}{110(0.950)} = \boxed{25.3 \text{ A}}$

P33.54 For the filter circuit,  $\frac{\Delta V_{\text{out}}}{\Delta V_{\text{in}}} = \frac{X_C}{\sqrt{R^2 + X_C^2}}$ .


(a) At  $f = 600 \text{ Hz}$ ,  $X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi(600 \text{ Hz})(8.00 \times 10^{-9} \text{ F})} = 3.32 \times 10^4 \Omega$

and  $\frac{\Delta V_{\text{out}}}{\Delta V_{\text{in}}} = \frac{3.32 \times 10^4 \Omega}{\sqrt{(90.0 \Omega)^2 + (3.32 \times 10^4 \Omega)^2}} \approx \boxed{1.00}$ .

(b) At  $f = 600 \text{ kHz}$ ,  $X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi(600 \times 10^3 \text{ Hz})(8.00 \times 10^{-9} \text{ F})} = 33.2 \Omega$

and  $\frac{\Delta V_{\text{out}}}{\Delta V_{\text{in}}} = \frac{33.2 \Omega}{\sqrt{(90.0 \Omega)^2 + (33.2 \Omega)^2}} = \boxed{0.346}$ .

**P33.56** The equation for  $\Delta v(t)$  during the first period (using  $y = mx + b$ ) is:

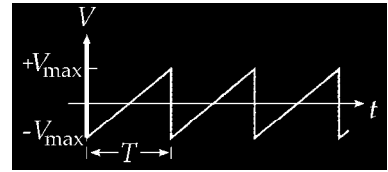

**FIG. P33.56**

$$\Delta v(t) = \frac{2(\Delta V_{\max})t}{T} - \Delta V_{\max}$$

$$[(\Delta v)^2]_{\text{ave}} = \frac{1}{T} \int_0^T [\Delta v(t)]^2 dt = \frac{(\Delta V_{\max})^2}{T} \int_0^T \left[ \frac{2}{T}t - 1 \right]^2 dt$$

$$[(\Delta v)^2]_{\text{ave}} = \frac{(\Delta V_{\max})^2}{T} \left( \frac{T}{2} \right) \left[ \frac{2t/T - 1}{3} \right]^3 \Bigg|_{t=0}^{t=T} = \frac{(\Delta V_{\max})^2}{6} [(+1)^3 - (-1)^3] = \frac{(\Delta V_{\max})^2}{3}$$

$$\Delta V_{\text{rms}} = \sqrt{[(\Delta v)^2]_{\text{ave}}} = \sqrt{\frac{(\Delta V_{\max})^2}{3}} = \frac{\Delta V_{\max}}{\sqrt{3}}$$

**P33.62** (a) With both switches closed, the current goes only through generator and resistor.

$$i(t) = \frac{\Delta V_{\max}}{R} \cos \omega t$$

(b)

$$(c) \quad i(t) = \frac{\Delta V_{\max}}{\sqrt{R^2 + \omega^2 L^2}} \cos \left[ \omega t + \arctan \left( \frac{\omega L}{R} \right) \right]$$

(d) For  $0 = \phi = \arctan \left( \frac{\omega_0 L - (1/\omega_0 C)}{R} \right)$ .

$$\text{We require } \omega_0 L = \frac{1}{\omega_0 C}, \text{ so } C = \frac{1}{\omega_0^2 L}.$$

(e) At this resonance frequency,  $Z = R$ .

$$(f) \quad U = \frac{1}{2} C (\Delta V_C)^2 = \frac{1}{2} C I^2 X_C^2$$


$$U_{\max} = \frac{1}{2} C I_{\max}^2 X_C^2 = \frac{1}{2} C \frac{(\Delta V_{\max})^2}{R^2} \frac{1}{\omega_0^2 C^2} = \frac{(\Delta V_{\max})^2 L}{2R^2}$$

$$(g) \quad U_{\max} = \frac{1}{2} L I_{\max}^2 = \frac{1}{2} L \frac{(\Delta V_{\max})^2}{R^2}$$

(h) Now  $\omega = 2\omega_0 = \frac{2}{\sqrt{LC}}$ .

$$\text{So } \phi = \arctan \left( \frac{\omega L - (1/\omega C)}{R} \right) = \arctan \left( \frac{2\sqrt{L/C} - (1/2)\sqrt{L/C}}{R} \right) = \arctan \left( \frac{3}{2R} \sqrt{\frac{L}{C}} \right).$$

(i) Now  $\omega L = \frac{1}{\omega C}$   $\omega = \frac{1}{\sqrt{2LC}} = \frac{\omega_0}{\sqrt{2}}$ .

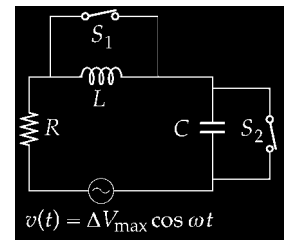

**FIG. P33.62**