

SPS tutoring  
 2321 Sterling  
 MW 9:55, 1:20, 2:25  
 TR 11  
 F 9:55, 1:20

### Capacitance

1st parallel plates



$$E = \sigma / \epsilon_0 \quad \sigma = \frac{\text{charge}}{\text{area}} \text{ on either plate}$$

$$E = \frac{V_a - V_b}{d}$$

$$\Rightarrow \frac{\sigma}{\epsilon_0} = \frac{V_{ab}}{d}$$

charge on plate =  $\sigma A$  ← plate area

$$Q = A\sigma = A \left( \frac{V_{ab} \epsilon_0}{d} \right)$$

$$Q = \left( \frac{A \epsilon_0}{d} \right) V_{ab} \Rightarrow C = \frac{\epsilon_0 A}{d} \text{ capacitance}$$



2 conductors

potential difference

$$\Delta V \propto Q$$

$$\Delta V = Q/C$$

$$Q = C \Delta V \text{ capacitance}$$

Capacitance relates

$Q$  (charge) to  $\Delta V$  (voltage difference)

depends on geometry.

but not on  $Q$  (or  $\Delta V$ )

unit of capacitance is Farad (F)

$$1 \text{ F} = 1 \text{ C/V}$$

F is big unit

typical capacitors range from

$10^{-12}$  F (pF) to  $10^{-6}$  F (μF)

parallel plates


$$C = \epsilon_0 A/d$$

Ex 2 concentric spheres.

find  $C$

given  $+Q, -Q$

find  $\Delta V$

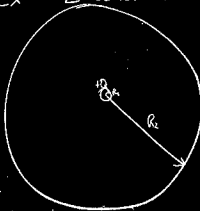

Field between  
 $R_1 + R_2$  is  
 $kQ/r^2$

everywhere  
else, field = 0

spheres

$$\Delta V = \int_{R_2}^{R_1} \frac{kQ}{r^2} = \frac{kQ}{R_1} - \frac{kQ}{R_2}$$

$$C = \frac{Q}{\Delta V} = \frac{1}{(k/R_1 - k/R_2)}$$

can also say  
total potential is sum of  
potentials from spheres 1 + 2

$$V_1 = \frac{kQ}{R_1} - \frac{kQ}{R_2} \Rightarrow V_1 - V_2 = \Delta V = kQ \left( \frac{1}{R_1} - \frac{1}{R_2} \right)$$
$$V_2 = 0$$


As  $R_2 \rightarrow 0$   
 $C \rightarrow \frac{R_1}{k}$

"capacitance of sphere"

Combining capacitances  
(in a circuit)

- series
- parallel

## Symbols

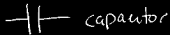

capacitor



battery



switch

capacitors




series



parallel

parallel

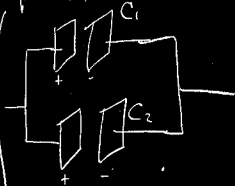

Voltage drop across  
 $C_1 + C_2$  is same ( $\Delta V$ )

need to find charge

$$Q_1 = C_1 \Delta V$$

$$Q_2 = C_2 \Delta V$$

---

$$\underbrace{Q_1 + Q_2}_{Q} = (C_1 + C_2) \Delta V$$

$$\text{so } Q = C_{\text{equiv}} \Delta V$$

$$C_{\text{equiv}} = C_1 + C_2$$



$\Delta V$  same across all  $C_i$

$$Q_1 = C_1 \Delta V$$


$$Q_2 = C_2 \Delta V$$

$$Q_N = C_N \Delta V$$

$$Q = \sum_{i=1}^N Q_i = \left( \sum_{i=1}^N C_i \right) \Delta V$$

$$C_{\text{equiv}} = \sum_{i=1}^N C_i$$


### Capacitors in series

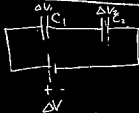

$$\Delta V_1 + \Delta V_2 = \Delta V$$

charges on capacitors are equal

Charge on 2 capacitors is same

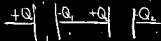

isolated, so  
 $-Q_1 + Q_2 = 0$

$$\Delta V_1 + \Delta V_2 = \Delta V$$

$$\frac{Q}{C_1} + \frac{Q}{C_2} = \Delta V$$

$$\frac{Q}{C_{eq}} = \frac{Q}{C_1} + \frac{Q}{C_2}$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$\text{or } C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

for  $N$  capacitors in series,

$$\sum_{i=1}^N \Delta V_i = \Delta V$$

all charges same,

$$\sum_{i=1}^N \frac{Q}{C_i} = \Delta V$$

$$\Rightarrow \frac{1}{C_{equiv}} = \sum_{i=1}^N \frac{1}{C_i}$$

$$\frac{1}{C_{eq}} = \frac{1}{8} + \frac{1}{8}$$
$$= \frac{1}{4}$$

if different combinations,  
just do step by step

