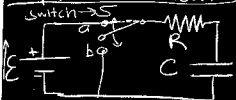


Capacitors in Circuits



RC circuit:

Switch at position a

Conservation of Energy.

Charge travels around circuit

In Δt , $Q = I \Delta t$ travels

thru circuit.

Work by EMF: $\Delta W = \epsilon \Delta Q$

must equal energy dissipated
in R ($I^2 R \Delta t$) PLUS

energy stored in
Capacitor ($\frac{Q \Delta Q}{C}$)

$$\epsilon \Delta Q = I^2 R \Delta t + \frac{Q \Delta Q}{C}$$

Divide by Δt

$$\epsilon \frac{\Delta Q}{\Delta t} = I^2 R + \frac{Q \Delta Q}{C \Delta t}$$

$$I = \frac{\Delta Q}{\Delta t} \Rightarrow$$

$$\epsilon I = I^2 R + I \frac{Q}{C} \Rightarrow \div I$$

If use loop theorem and
remember $V_{cap} = \frac{Q}{C}$

$$\boxed{\epsilon - IR - \frac{Q}{C} = 0}$$

around Loop

$$\epsilon = IR + \frac{Q}{C}, I = \frac{\Delta Q}{\Delta t}$$

$$\epsilon = \frac{\Delta Q}{\Delta t} R + \frac{Q}{C}, \text{ use differentials}$$

$$\epsilon = \frac{dQ}{dt} R + \frac{Q}{C}$$

divide by R

$$\frac{dQ}{dt} = \frac{\mathcal{E}}{R} - \frac{Q}{RC} = -\frac{1}{RC} (Q - C\mathcal{E})$$

Integrate
 $q: 0 \rightarrow Q$
 $t: 0 \rightarrow t$

$$\frac{dQ}{Q - C\mathcal{E}} = -\frac{dt}{RC}$$

$$\int_0^Q \frac{dq}{q - C\mathcal{E}} = -\int_0^t \frac{dt}{RC}$$

$$\ln\left(\frac{Q - C\mathcal{E}}{-C\mathcal{E}}\right) = -\frac{t}{RC}$$

Exponential both sides

$$\frac{Q - C\mathcal{E}}{-C\mathcal{E}} = e^{-t/RC} \Rightarrow Q = C\mathcal{E}(1 - e^{-t/RC})$$


Let final charge = $Q_f = C\mathcal{E}$, $Q = Q_f(1 - e^{-t/RC})$

Current = $i = \frac{dQ}{dt} = \frac{\mathcal{E}}{R} e^{-t/RC} = I_0 e^{-t/RC}$

Let $I_0 = \frac{\mathcal{E}}{R}$ = initial current

at $t=0$: $Q=0$, $I = I_0 = \mathcal{E}/R$

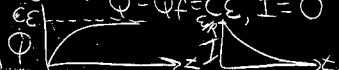at $t=\infty$: $Q = Q_f = C\mathcal{E}$, $I = 0$



Voltage across C
 $Q = CV$
 $V = Q/C$

"time to charge" given by product RC has dimensions of time ϵ = time for capacitor to reach $(1 - e^{-1}) = 63\%$ of its final value
 $Q = CE(1 - e^{-RC/t}) = CE(1 - e^{-1}) = 0.63 CE$
 for $t = RC$, Typical values, $C = 1.0 \mu F$, $R = 2000 \Omega$

$RC = 2 \times 10^{-3}$ secs
 Back to circuit + after long time: $t \gg RC$
 move switch $(a) \rightarrow (b)$
 No EMF in circuit



Loop: $IR + \frac{Q}{C} = 0$

$I = \frac{dQ}{dt} \Rightarrow R \frac{dQ}{dt} + \frac{Q}{C} = 0$

$R \frac{dQ}{dt} = -\frac{Q}{C} \Rightarrow \frac{dQ}{dt} = -\frac{Q}{RC} \Rightarrow$

$\frac{dQ}{Q} = -\frac{dt}{RC} \Rightarrow$ Integrate $q: Q_0 \rightarrow Q$

$Q_0 = CE$ ← starting charge during $t: 0 \rightarrow t$ was Q (at end of pt. 1)

$\int_{Q_0}^Q \frac{dq}{q} = -\frac{1}{RC} \int_0^t dt$

$\ln\left(\frac{Q}{Q_0}\right) = -\frac{t}{RC} \Rightarrow Q = Q_0 e^{-t/RC}$

$$i = \frac{dQ}{dt} = -\frac{Q_0}{RC} e^{-t/RC}$$

$$= I_0 e^{-t/RC}$$

$$I_0 = Q_0/RC$$

Initial Voltage across Cap = $\frac{Q_0}{C} = \mathcal{E}$

At start (switch at ⓐ)

$$Q_0 = C\mathcal{E}, \text{ after time } t = RC$$

$$Q = Q_0 e^{-RC/RC}$$

$$= Q_0 e^{-1} = 0.37 Q_0$$

time $t = RC$ is the time to reduce charge to 37% of its original value

Current $I = \frac{Q}{RC} e^{-t/RC}$

$$Q_0 = C\mathcal{E}; I = \frac{RC}{RC} \frac{\mathcal{E}}{R} e^{-t/RC}$$

Current starts at $\mathcal{E}/R \rightarrow$ decreases

Energy: Charging (switch at ⓐ)

Battery delivers Power $\mathcal{E}i$

Energy dissipated in R: $i^2 R$

Energy stored in Cap: iQ (Cap Voltage)

$$\Sigma i = i^2 R + iQ/C$$

Total Energy supplied = $\mathcal{E}Q_f$ (by Battery)

Total Energy Stored in Cap = $\frac{1}{2} \mathcal{E}Q_f$ (final Vltz on Cap)


Total energy dissipated in R is rest: $= \mathcal{E}Q_f - \frac{1}{2} \mathcal{E}Q_f = \frac{1}{2} \mathcal{E}Q_f$

$\frac{1}{2}$ energy stored in Cap.
 $\frac{1}{2}$ energy dissipated in R


How do we measure currents + voltages?

Measure current in wire
 → break wire + insert an Ammeter: $\text{---} \textcircled{A} \text{---}$
 all current flows thru it
 → Resistance of Ammeter must be small or changes current.

Example Measuring Circuit

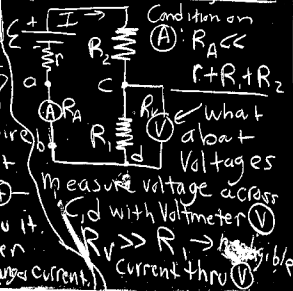

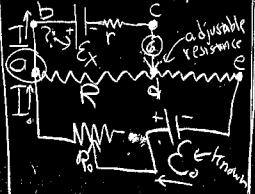How to measure EMF (not voltage output) Potentiometer + balance Voltages so no substantial current flows thru EMF



(G) = Galvanometer
= very \pm current meter

Loop theorem

$$-E_x - I r + (I_0 - I) R = 0$$

$I_0 - I$ = current in Big Resistor R

Junction Theorem at a

$$I = \frac{I_0 R - E_x}{R + r}$$

→ till equals value R_x

$$I_0 R_x = E_x$$