

Inductance of Solenoid
 (oo-long) piece of length l
 N turns per length,
 cross section area A

$$L = \frac{N \Phi_B}{I} = \frac{N}{I} B = \boxed{\mu_0 N^2 l A}$$

Proportional to Volume = lA
 and N^2 - double turns:
 # turns doubles, flux thru each
 doubles $\rightarrow \times 4 \Rightarrow N^2$

Inductor w/ Current I
 Changing $dI/dt \Rightarrow$

$$\mathcal{E} = L dI/dt$$

$$\text{Power: } P = \mathcal{E} I$$

$$= L \left(\frac{dI}{dt} \right) I =$$

$$P = L I dI/dt$$

Supply energy in dt:

$$dW = P dt$$

$$dW = L I \left(\frac{dI}{dt} \right) dt = L I dI$$

Work to increase current: $0 \rightarrow I$

$$W = \int_0^I L I dI = L \int_0^I I dI = \frac{1}{2} L I^2$$

Inductor L w/ current I

$$\text{has stored energy } U_B = \frac{1}{2} L I^2$$

Analogous to energy stored

In a capacitor C w/ charge Q

$$U_E = \frac{1}{2} \frac{Q^2}{C}$$

Energy density of magnetic field = Energy / Volume

Energy stored in Solenoid

area A, length l \Rightarrow Volume = Al

Uniform B \Rightarrow Energy is uniform

$$\frac{\text{Energy}}{\text{Volume}} = \frac{U_B}{\text{Vol}}; U_B = \frac{U_B}{Al} = \frac{1}{2} LI^2$$

$$L \text{ for Solenoid} = \mu_0 N^2 A l$$

$$U_B = \frac{1}{2} \frac{(\mu_0 N^2 A l) I^2}{Al} = \frac{1}{2} \mu_0 N^2 I^2$$

Inside Solenoid

$$B = \mu_0 I n \Rightarrow$$


$$I = B / \mu_0 N$$

$$U_B = \frac{1}{2} \mu_0 N^2 \left(\frac{B}{\mu_0 N} \right)^2$$

$$U_B = \frac{1}{2} \frac{B^2}{\mu_0} \quad \begin{array}{|c|} \hline \text{energy} \\ \text{per unit} \\ \text{Volume} \\ \hline \end{array}$$

$$U_E = \frac{1}{2} \epsilon_0 E^2$$

Circuit w/ R and L

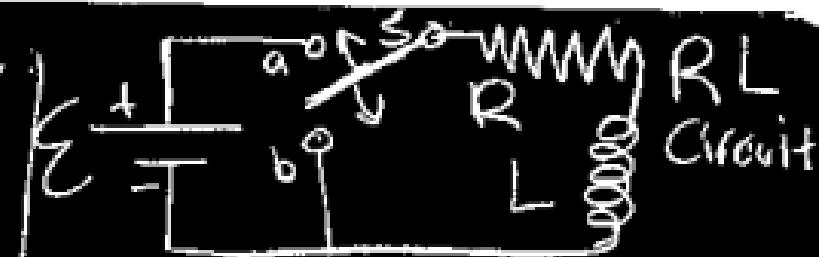

Close switch \rightarrow current I in Resistor increases
w/o L $\Rightarrow I = E/R$

w/ L \Rightarrow self-induced E_L

L en? \Rightarrow opposes increase in I
 \Rightarrow opposes battery E

Resistor sees $\approx \epsilon_j$; (E, E_L) inductor

$\mathcal{E}_L = -L \frac{dI}{dt}$. Switch at position a:

Loop Theorem: $\sum V = 0$
 $\mathcal{E} - IR - L \frac{dI}{dt} = 0$

$X \rightarrow Y: V_R = -IR$
 $Y \rightarrow Z: V_L = -L \frac{dI}{dt}$
 $Z \rightarrow X: \mathcal{E}$

$-IR - L \frac{dI}{dt} + \mathcal{E} = 0$
 $\mathcal{E} = L \frac{dI}{dt} + IR$

$\frac{dI}{dt} = \frac{\mathcal{E} - IR}{L} = \frac{\mathcal{E}}{L} - \frac{R}{L} I$

When close switch ($t=0$)
 $I=0 \Rightarrow \left. \frac{dI}{dt} \right|_{t=0} = \frac{\mathcal{E}}{L}$

$at t=\infty \Rightarrow \frac{dI}{dt} = 0$
 $0 = \frac{\mathcal{E}}{L} - \frac{R}{L} I \Rightarrow I = \frac{\mathcal{E}}{R}$

$I = \frac{\mathcal{E}}{R} (1 - e^{-\frac{Rt}{L}})$

$\frac{dI}{dt} = \frac{\mathcal{E} - RI}{L} = \frac{\mathcal{E}}{L} - \frac{R}{L} I$

$\frac{dI}{dt} = \frac{\mathcal{E}}{L} e^{-\frac{Rt}{L}}$ is derivative of I when plugged in

Capacitance: $e^{-t/RC}$
 \Rightarrow characteristic time:
 $t_c = RC$

Inductance: $e^{-Rt/L}$
 \Rightarrow characteristic time
 $(L = \frac{1}{R})$ dimensions of time

$$\text{Plug in } t_L = L/R$$

$$I = \frac{\mathcal{E}}{R} (1 - e^{-t_L}) = \frac{63\mathcal{E}}{R}$$


time at which current rises to 63% of final value.

After long time.. open switch to position b $\Rightarrow \mathcal{E} = 0$

$$\text{Loop: } L \frac{dI}{dt} + IR = 0$$

$$I = \frac{\mathcal{E}}{R} e^{-t/t_L} = \frac{\mathcal{E}}{R} e^{-Rt/L}$$

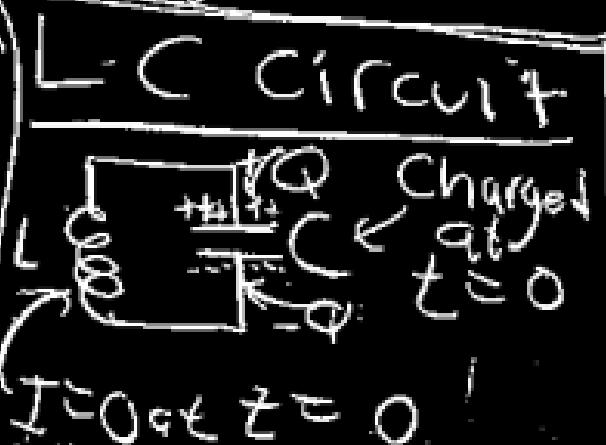t_L = time for current to decay to 37% of its original value.
energy to maintain current when $\mathcal{E} = 0$ is Energy stored in magnetic field



at $t = 0$ Energy stored in C
 $U_E = \frac{1}{2} \frac{Q^2}{C}$, $U_B = \frac{1}{2} LI_s^2 = 0$

Capacitor discharges thru Inductor L \Rightarrow Current I from $\frac{dQ}{dt} = I$, as charge in C decreases, U_E decreases, current in L increases \Rightarrow U_B increases $\Rightarrow Q = 0$ and $U_E = \frac{1}{2} \frac{Q^2}{C} = 0$, $U_B = \frac{1}{2} LI^2$

<p>Oscillating system with frequency f $\omega = 2\pi f$ analogous to mass on spring mass m, spring const. k</p>	<p>Spring: $U = \frac{1}{2} k x^2$ $U_E = \frac{1}{2} \left(\frac{1}{c}\right) q_h^2$</p>	$U = \frac{1}{2} L i^2 + \frac{1}{2} \frac{q_h^2}{c}$. Solve for i . At $t=0$ $q_h = Q$, $i=0$ $U = \frac{1}{2} L i^2 + \frac{1}{2} \frac{q_h^2}{c} = \frac{Q^2}{2c}$
<p>Charge q_h corresponds to displacement x Current $i = \frac{dq_h}{dt}$ gives: $V = \frac{dx}{dt}$ C corresponds to $\frac{1}{k}$, L corresponds to m</p>	<p>Mass: $KE = \frac{1}{2} m V^2$ $U_B = \frac{1}{2} L I^2$ Frequency $\omega = \sqrt{\frac{k}{m}}$ LC circuit: $\omega = \frac{1}{\sqrt{LC}}$</p>	<p>Energy Cons. (no R) True for all time: $i = \sqrt{\frac{1}{LC} (Q^2 - q_h^2)}$ Reminds: $V = \pm \omega \sqrt{A^2 x^2}$</p>

$$V = \frac{dX}{dt} \Leftrightarrow i = \frac{dq_h}{dt}$$

$$X = A \cos \omega t \Rightarrow$$

$$q_h = Q \cos \omega t$$

$$\text{where } \omega = \frac{1}{\sqrt{LC}}$$

$$q_h = Q \cos \sqrt{\frac{1}{LC}} t$$

If we add resistance

$$U = \frac{1}{2} L i^2 + \frac{1}{2} \frac{q_h^2}{C}$$

$$\frac{dU}{dt} = - i^2 R \in \begin{matrix} \text{Power} \\ \text{Loss} \end{matrix} \text{ in } R$$

$$L i \frac{di}{dt} + \frac{q_h}{C} \frac{dq_h}{dt} = - i^2 R$$

$$i = \frac{dq_h}{dt} \Rightarrow \frac{di}{dt} = \frac{d^2 q_h}{dt^2}$$

Divide by $i \Rightarrow$

$$L \frac{d^2 q_h}{dt^2} + R \frac{dq_h}{dt} + \frac{q_h}{C} = 0$$

$$q_h = Q e^{-Rt/2L} \cos(\omega t + \phi)$$

$$\omega' = \sqrt{\omega^2 - (R/2L)^2}$$

$$\omega = \frac{1}{\sqrt{LC}}$$