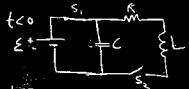


202 Exam
 Wed Mar 16
 5:45-6:45 pm

§32 RLC circuit



$t=0$
 open S_1 & close S_2



find $Q(t)$
 $[I(t) = \frac{dQ(t)}{dt}]$

$$\sum \text{voltage drops} = 0$$

$$\text{voltage across } C = Q/C$$

$$\text{voltage across } R = IR$$

$$\text{" " } L = L \frac{dI}{dt}$$

$$\text{note also } I = \frac{dQ}{dt}$$

$$L \frac{dI}{dt} + IR + \frac{Q}{C} = 0$$

$$L \frac{d^2Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} = 0$$

same eqn as damped harmonic oscillator

if resistance large,

$$Q(t) = Q_0 e^{-\Gamma t}$$

$$\frac{dQ(t)}{dt} = -\Gamma Q_0 e^{-\Gamma t}$$

$$\frac{d^2Q(t)}{dt^2} = \Gamma^2 Q_0 e^{-\Gamma t}$$

plug into differential equation

$$L \Gamma^2 Q_0 e^{-\Gamma t} - R \Gamma Q_0 e^{-\Gamma t} + \frac{1}{C} Q_0 e^{-\Gamma t} = 0$$

$$\Gamma^2 - \frac{R}{L} \Gamma + \frac{1}{LC} = 0$$

$$\Gamma = \frac{1}{2} \frac{R}{L} \left(1 \pm \sqrt{1 - \frac{4L}{R^2 C}} \right)$$

Final and solution is constant as long as

$$R^2 > 4/LC$$

"critical resistance"

$$R_c = \sqrt{4/LC}$$

if $R < R_c$


result.

$$Q(t) = Q(t=0) e^{-Rt/2L} \cos \omega t$$


$$\omega = \left[\frac{1}{LC} - \left(\frac{R}{2L} \right)^2 \right]^{1/2}$$

$R > R_c$

Q

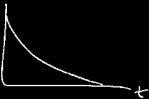

$R < R_c$

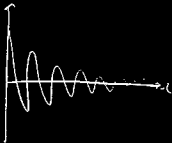

§ 33 AC circuits

Consider sinusoidal drive

§ 33.2 resistor




AC voltage $\Delta V_R = \Delta V_{max} \sin \omega t$

$$\text{current } i_R = \frac{\Delta V_R}{R} = \frac{\Delta V_{max}}{R} \sin \omega t$$

So $i_R = I_{max} \sin \omega t$
with $I_{max} = \frac{\Delta V_{max}}{R}$

$$\Delta V_R = I_{max} R \sin \omega t$$

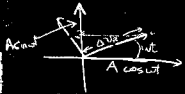

Power dissipated in resistor


$$P(t) = i^2 R = I_{max}^2 \sin^2 \omega t R$$

average power = $R \langle I^2(t) \rangle = R \left(\frac{1}{T} \int_0^T I_{max}^2 \sin^2(\omega t) dt \right) = R \left(\frac{1}{2\pi} \int_0^{2\pi} I_{max}^2 \sin^2(\omega t) d(\omega t) \right) = R \left(\frac{1}{2\pi} \right) \left(\frac{2\pi}{\omega} \right) I_{max}^2 = \frac{1}{2} I_{max}^2 R$

Define RMS current
 $I_{rms} = I_{max} / \sqrt{2}$
 $P = I_{rms}^2 R$

§33.3 Inductor in ac circuit

consider circuit

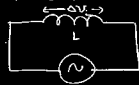

$$\Delta V_L = \Delta V_{max} \sin \omega t$$

$$\Delta V_L = \mathcal{E}_L = -L \frac{di}{dt}$$

$$\Delta V_{max} \sin \omega t - L \frac{di}{dt} = 0$$

$$di = \frac{\Delta V_{max}}{L} \sin \omega t dt$$

integrate:

$$i = -\frac{\Delta V_{max}}{\omega L} \cos \omega t (+C)$$


0 if any resistance at all

$$i = -\frac{\Delta V_{\max}}{\omega L} \cos \omega t$$

$$= -\frac{\Delta V_{\max}}{\omega L} \left[-\sin \left(\omega t - \frac{\pi}{2} \right) \right]$$

$$i(t) = \frac{\Delta V_{\max}}{\omega L} \sin \left(\omega t - \frac{\pi}{2} \right)$$

current lags voltage

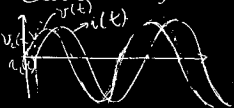

current lags voltage by $\pi/2$
(1/4 of cycle)

Note: max current $I_{\max} = \frac{\Delta V_{\max}}{\omega L}$

Define $\frac{\Delta V_{\max}}{\Delta I_{\max}} = \omega L \equiv X_L$ inductive reactance

$$I_{\max} = \frac{\Delta V_{\max}}{X_L} \quad \left[\text{analogy with resistor: } I_{\max} = \frac{\Delta V_{\max}}{R} \right]$$



§ 33.4 Cap actors in an AC circuit



$$\Delta V = \Delta V_{\max} \sin \omega t$$

Kirchhoff's voltage law

$$\Delta V_C = \Delta V = \Delta V_{\max} \sin \omega t$$



Since $q = C \Delta V_C$

$$q = C \Delta V_{\max} \sin \omega t$$

current $i_C = \frac{dq}{dt} = C \Delta V_{\max} \omega \cos \omega t = \omega C \Delta V \sin(\omega t + \pi/2)$

$$i_C = \omega C \Delta V \sin(\omega t + \pi/2)$$

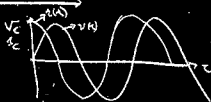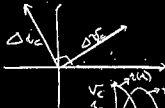
current leads voltage (capactor) by $\pi/2$



$$I_{\max} = \frac{\Delta V_{\max}}{(1/\omega C)}$$

capacitive reactance $X_C = \frac{1}{\omega C}$
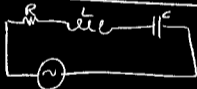
$$\Rightarrow I_{\max} = \frac{\Delta V_{\max}}{X_C}$$



$$\Delta V = \Delta V_{\max} \sin \omega t$$

Current $i = I_{\max} \sin(\omega t - \phi)$
need to find I_{\max} and ϕ