



$$\Delta v = \Delta V_{\max} \sin \omega t$$

current $i = I_{\max} \sin(\omega t - \phi)$
find I_{\max} , ϕ

$$\Delta v_R = I_{\max} R \sin(\omega t - \phi) = \Delta V_R \sin(\omega t - \phi) \quad [\Delta V_R = I_{\max} R]$$

$$\Delta v_L = I_{\max} X_L \sin(\omega t - \phi + \pi/2) = \Delta V_L \cos(\omega t - \phi) \quad [\Delta V_L = I_{\max} X_L] \quad X_L = \omega L$$

$$\Delta v_C = I_{\max} X_C \sin(\omega t - \phi - \pi/2) = -\Delta V_C \cos(\omega t - \phi) \quad [\Delta V_C = I_{\max} X_C] \quad X_C = \frac{1}{\omega C}$$

$$\Delta v_R + \Delta v_L + \Delta v_C = \Delta v \quad [\text{Kirchhoff voltage}]$$

$$I_{\max} R \sin(\omega t - \phi) + I_{\max} X_L \cos(\omega t - \phi) - I_{\max} X_C \cos(\omega t - \phi) = \Delta V_{\max} \sin \omega t$$

Use $\sin(x-y) = \sin x \cos y - \cos x \sin y$ $\cos(x-y) = \cos x \cos y + \sin x \sin y$

$$\begin{aligned}
 & I_{\max} R (\sin \omega t \cos \phi - \cos \omega t \sin \phi) \\
 & + I_{\max} X_L (\cos \omega t \cos \phi + \sin \omega t \sin \phi) \\
 & - I_{\max} X_C (\cos \omega t \cos \phi + \sin \omega t \sin \phi) \\
 & = \Delta V_{\max} \sin \omega t
 \end{aligned}$$

Solve ① + ② \Rightarrow

$$I_{\max} = \frac{\Delta V_{\max}}{\sqrt{R^2 + (X_L - X_C)^2}}$$

$$\tan \phi = \frac{X_L - X_C}{R}$$

$$X_L = \omega L \quad X_C = \frac{1}{\omega C}$$

define impedance

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\Delta V_{\max} = I_{\max} Z$$

$$\begin{aligned}
 & \sin \omega t (I_{\max} R \cos \phi + I_{\max} X_L \sin \phi - I_{\max} X_C \sin \phi - \Delta V_{\max}) \\
 & + \cos \omega t (-I_{\max} R \sin \phi + I_{\max} X_L \cos \phi - I_{\max} X_C \cos \phi) = 0
 \end{aligned}$$



true for all times \Rightarrow

① $I_{\max} R \cos \phi + I_{\max} X_L \sin \phi - I_{\max} X_C \sin \phi - \Delta V_{\max} = 0$ AND

② $-I_{\max} R \sin \phi + I_{\max} X_L \cos \phi - I_{\max} X_C \cos \phi = 0$

Resonance in RLC circuit

$$\text{calculate } I_{RMS} = \frac{\Delta V_{RMS}}{\sqrt{R^2 + (X_L - X_C)^2}}$$

$$\text{max. } I_{RMS} \text{ is } \frac{\Delta V_{RMS}}{R} \quad \begin{matrix} (X_L = \omega L) \\ (X_C = 1/\omega C) \end{matrix}$$

$$\text{when } X_L = X_C$$

Resonance condition

$$\omega L = \frac{1}{\omega C}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

§ 33.6 Power in ac circuit

instantaneous power supplied is $I \cdot V$

$$\begin{aligned} P &= i \Delta v = I_{max} \sin(\omega t - \phi) \Delta V \sin \omega t \\ &= I_{max} \Delta V_{max} \sin \omega t \sin(\omega t - \phi) \end{aligned}$$

time average of power:

$$\begin{aligned} \bar{P} &= I_{max} \Delta V_{max} \sin \omega t [\sin \omega t \cos \phi - \cos \omega t \sin \phi] \\ &= I_{max} \Delta V_{max} [\sin^2 \omega t \cos \phi - \sin \omega t \cos \omega t \sin \phi] \\ &= I_{max} \Delta V_{max} \left\{ \underbrace{\frac{1}{2} \cdot \frac{1}{2} \sin 2\omega t}_{\text{time average} = 0} \cos \phi - \frac{1}{2} \sin \underbrace{2\omega t}_{\text{time average} = 0} \sin \phi \right\} \end{aligned}$$

$$P = \frac{I_{max} \Delta V_{max}}{2} \cos \phi$$

$$\bar{P} = I_{rms} \Delta V_{rms} \cos \phi$$

all power is dissipated in R.

max voltage drop across R is $I_{max} R$

$$I_{max} = \frac{\Delta V_{max}}{\sqrt{R^2 + (X_L - X_C)^2}} = \frac{\Delta V_{max}}{R} \frac{R}{\sqrt{R^2 + (X_L - X_C)^2}}$$

$$= \frac{\Delta V_{max}}{R} \cos \phi$$

So $I_{rms} \rightarrow \frac{\Delta V_{rms}}{R} \cos \phi$


$$\Delta V_{rms} \cos \phi = I_{rms} R$$

$$\text{and } I_{rms} \Delta V_{rms} \cos \phi = I_{rms}^2 R$$

Calculate power as function of ω :

$$P_{AVE} = \frac{(\Delta V_{rms})^2 R}{Z^2} = \frac{(\Delta V_{rms})^2 R}{R^2 + (X_L - X_C)^2}$$
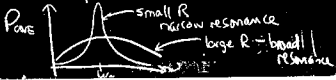
$$P_{AVE} = \frac{(\Delta V_{rms})^2 R \omega^2}{R^2 \omega^2 + L^2 (\omega^2 - \omega_0)^2} \quad [\omega_0 = 1/\sqrt{LC}]$$



Max power dissipated when $\omega = \omega_0$

$$P_{\text{max}} = \frac{(\Delta V_{\text{rms}})^2 R \omega_0^2}{R^2 \omega_0^2} = \frac{(\Delta V_{\text{rms}})^2}{R}$$

Peak described by quality factor Q

$$Q = \frac{\omega_0}{\Delta \omega}$$

$\Delta \omega =$ width at half-power

$$\Delta \omega = R/L$$

So $Q = \omega_0 L/R$

high $Q \rightarrow$ response at resonant frequency



§33.8 transformers
& power transmission

fixed power delivered
to a load P_{AV}


$$I_{\text{rms}} = \frac{P_{\text{AV}}}{\Delta V_{\text{rms}}}$$

power dissipated in resistor R

$$= \left(\frac{P_{\text{AV}}}{\Delta V_{\text{rms}}} \right)^2 R$$

higher $\Delta V_{\text{rms}} \Rightarrow$ lower loss

AC transformer converts
high V to low V:

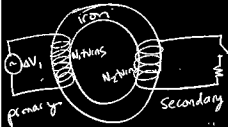

1st primary: Faraday:

$$\Delta V_1 = -N_1 \frac{d\Phi_B}{dt}$$

Φ_B magnetic flux
turns

secondary:

$$\Delta V_2 = -N_2 \frac{d\Phi_2}{dt}$$

$$\text{but } \Phi_1 = \Phi_2$$

$$\Rightarrow \Delta V_2 = \frac{N_2}{N_1} \Delta V_1$$

$$N_2 > N_1 \Rightarrow \Delta V_2 > \Delta V_1$$

"step-up transformer"

$$N_2 < N_1 \Rightarrow \Delta V_2 < \Delta V_1$$

"step-down transformer"