

AC Circuit Homework.

1) (a) $V(t) = I(t) \cdot R \Rightarrow V_{RMS} = I_{RMS} \cdot R$. Also we know
 $P = I_{RMS}^2 R = I_{RMS} \cdot V_{RMS}$

$I_{RMS} = P / V_{RMS} = 60W / 115V \Rightarrow \boxed{I_{RMS} = 0.52A}$

(b) $I_0 = \sqrt{2} I_{RMS} \Rightarrow \boxed{I_0 = 0.74A}$

(c) $P_{max} = I_0^2 R = (\sqrt{2} I_{RMS})^2 R = 2 I_{RMS}^2 R \Rightarrow \boxed{P_{max} = 120W}$

2) (a) $\omega = 2\pi f = 2\pi \cdot (60/s) \Rightarrow \boxed{\omega = 377/s}$

(b) $I_0 = V_0 / R = 20V / 3\Omega \Rightarrow \boxed{I_0 = 6.67A}$

$I_{RMS} = I_0 / \sqrt{2} \Rightarrow \boxed{I_{RMS} = 4.71A}$

(c) $P = (I_{RMS})^2 \cdot R = (4.71A)^2 \cdot 3\Omega \Rightarrow \boxed{P = 66.7W}$

3) (a) $X_L = \omega L$

$f = 60/s \Rightarrow \omega = 377/s \quad X_L = (377/s)(10^{-3}H) = \boxed{0.377\Omega}$

$f = 6 \times 10^3/s \quad \omega = 3.77 \times 10^4/s \quad \boxed{X_L = 37.7\Omega}$

(b) $X_C = 1 / \omega C$

$f = 60/s \Rightarrow X_C = [(377/s) \cdot (10^{-5}F)]^{-1} \Rightarrow \boxed{X_C = 265\Omega}$

$f = 6 \times 10^3/s \Rightarrow \boxed{X_C = 2.65\Omega}$

4) $X_L = \omega L = (2\pi) \cdot (60/s) \cdot (0.050) = 18.85\Omega$

For an LRC circuit, the impedance is $[R^2 + (X_L - X_C)^2]^{\frac{1}{2}}$

and so if there is no capacitor we have

$Z = [R^2 + X_L^2]^{\frac{1}{2}} = [(10\Omega)^2 + (18.85\Omega)^2]^{\frac{1}{2}} = 21.3\Omega$

$I_{RMS} = V_{RMS} / Z = (115V) / (21.3\Omega) \Rightarrow \boxed{I_{RMS} = 5.4A}$

5) The frequency we want is $f = 1050 \text{ kHz} = 1.05 \times 10^6 \text{ Hz}$
 $\Rightarrow \omega = 2\pi f = 6.6 \times 10^6 / \text{s}$

The resonant frequency is

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

\Rightarrow

$$LC = \frac{1}{\omega^2} = 2.3 \times 10^{-14} \text{ s}^2$$

If $L = 10^{-3} \text{ H}$ then

$$C = 2.3 \times 10^{-14} \text{ s}^2 / 10^{-3} = 2.3 \times 10^{-11} \text{ F}$$

$$\boxed{C = 23 \text{ pF}} \quad p = \text{pico} = 10^{-12}$$

b) (a) $U = \frac{1}{2} CV^2 = \frac{1}{2} (5 \times 10^{-6} \text{ F}) (30 \text{ V})^2 \Rightarrow \boxed{U = 2.25 \times 10^{-3} \text{ J}}$

(b) The natural oscillation frequency is

$$\omega = \frac{1}{\sqrt{LC}} = [(10^{-2} \text{ H})(5 \times 10^{-6} \text{ F})]^{-\frac{1}{2}} = 4472 / \text{s}$$

$$\boxed{\omega = 4472 / \text{s}} \quad \text{OR} \quad \boxed{f = \frac{\omega}{2\pi} = 712 \text{ Hz}}$$

(c) The energy is transferred back and forth between the capacitor and the inductor. The peak current occurs when $U_C = 0$
 then

$$U_L = \frac{1}{2} LI^2 = 2.25 \times 10^{-3} \text{ J}$$

$$I = [(2)(2.25 \times 10^{-3} \text{ J}) / (0.01 \text{ H})]^{1/2} \quad \boxed{I_{\text{max}} = 0.67 \text{ A}}$$

7) (a) We need to remember that for a capacitor, the voltage trails the current by 90° . We will also use


$$X_C = \frac{1}{\omega C} = \frac{1}{(3000 / \text{s})(5 \times 10^{-6} \text{ F})} = 66.7 \Omega$$

This tells us that

$$V_{0C} = X_C I_0 = 66.7 \Omega \cdot I_0$$

$$V_{0R} = I_0 \cdot R = 40 \Omega \cdot I_0$$

The phasor diagram is shown at the right

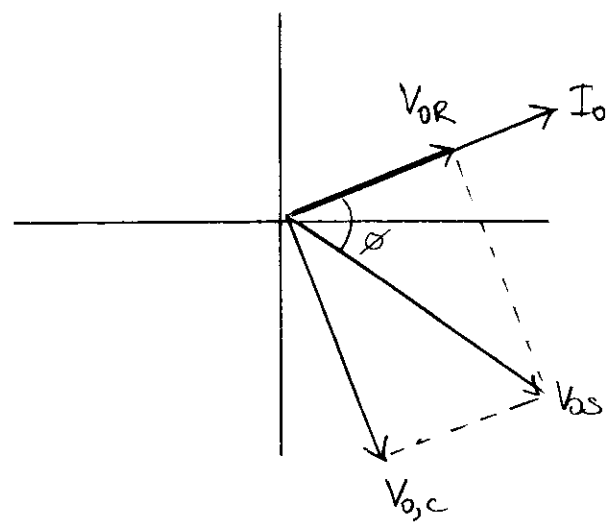



$$\begin{aligned}
 (b) \quad V_{0s} &= [V_{0R}^2 + V_{0c}^2]^{\frac{1}{2}} \\
 &= [(RI_0)^2 + (X_c I_0)^2]^{\frac{1}{2}} \\
 &= I_0 [R^2 + X_c^2]^{\frac{1}{2}}
 \end{aligned}$$

So

$$I_0 = (5V) / [(40\Omega)^2 + (66.7\Omega)^2]^{\frac{1}{2}} \quad \boxed{I_0 = 64\text{mA}}$$

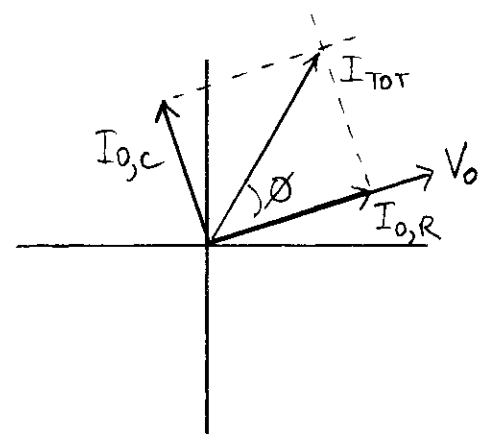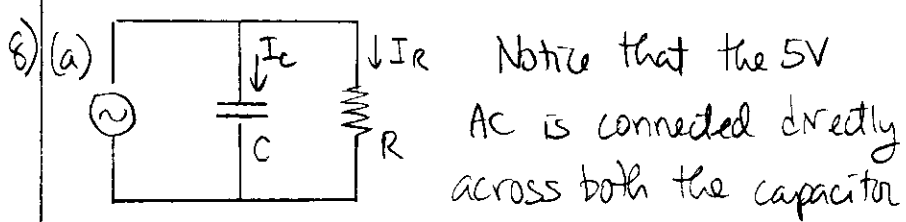(c) From the picture the current leads the voltage by an angle ϕ

where $\tan\phi = \frac{V_{0c}}{V_{0R}} = \frac{X_c}{R} = \frac{66.7\Omega}{40\Omega} \quad \boxed{\phi = 59^\circ}$



and the resistor, so we have

$$\begin{aligned}
 I_{0,c} &= 5V / X_c = 0.075A \\
 I_{0,R} &= 5V / R = 0.125A
 \end{aligned}$$

(b) From the drawing

$$I_0 = [(I_{0,c})^2 + (I_{0,R})^2]^{\frac{1}{2}} = [(75\text{mA})^2 + (125\text{mA})^2]^{\frac{1}{2}} \quad \boxed{I_0 = 146\text{mA}}$$

(c) Again the current leads the voltage, and the phase angle is ϕ where

$$\tan\phi = \frac{I_{0c}}{I_{0R}} = \frac{75}{125} = 0.6 \quad \boxed{\phi = 31^\circ}$$

9) (a) The resonant frequency is $\omega = \frac{1}{\sqrt{LC}}$

$$\omega = [(3 \times 10^{-9} \text{ F}) \cdot (5 \times 10^{-5} \text{ H})]^{-\frac{1}{2}} = \underline{2.582 \times 10^6 / \text{s}}$$

At the resonant frequency

$$X_C = X_L = \omega L = (2.582 \times 10^6 / \text{s})(5 \times 10^{-5} \text{ H}) = \underline{129 \Omega}$$

$$Z = [R^2 + (X_L - X_C)^2]^{\frac{1}{2}} = R = 5 \Omega$$

so

$$I_0 = 5 \text{ V} / 5 \Omega \quad \boxed{I_0 = 1 \text{ A}}$$

(b) Here $X_L = \omega L = (0.8) \omega_0 L = (0.8)(129 \Omega) = 103.2 \Omega$

$$X_C = \frac{1}{\omega C} = \frac{1}{0.8 \omega_0 C} = \left(\frac{1}{0.8}\right)(129 \Omega) = 161.2$$

$$Z = [R^2 + (X_L - X_C)^2]^{\frac{1}{2}} = [(5 \Omega)^2 + (103.2 \Omega - 161.2 \Omega)^2]^{\frac{1}{2}} = 58 \Omega$$

\Rightarrow

$$I_0 = 5 \text{ V} / 58 \Omega \quad \boxed{I_0 = 0.086 \text{ A}}$$

(c) At $1.2 \cdot \omega_0$

$$X_L = (1.2) \cdot (129 \Omega) = 154.8 \Omega$$

$$X_C = (129 \Omega) / 1.2 = 107.5$$

$$Z = 47.6 \Omega$$

$$\boxed{I_0 = 0.105 \text{ A}}$$